


# **18-447 Lecture 4: Single-Cycle Microarchitecture**

James C. Hoe  
Department of ECE  
Carnegie Mellon University

# Housekeeping



- Your goal today
  - first try at implementing the RV32I ISA
- Notices
  - Student survey on Canvas, **due Wednesday**
  - Handout #4: HW1, **due noon 2/7**
  - Lab 1, Part A, **due Week 3**
  - Lab 1, Part B, **due Week 4**
- Readings
  - P&H Ch 4.1~4.4
  - finish reading P&H Ch 2

# Instruction Processing FSM

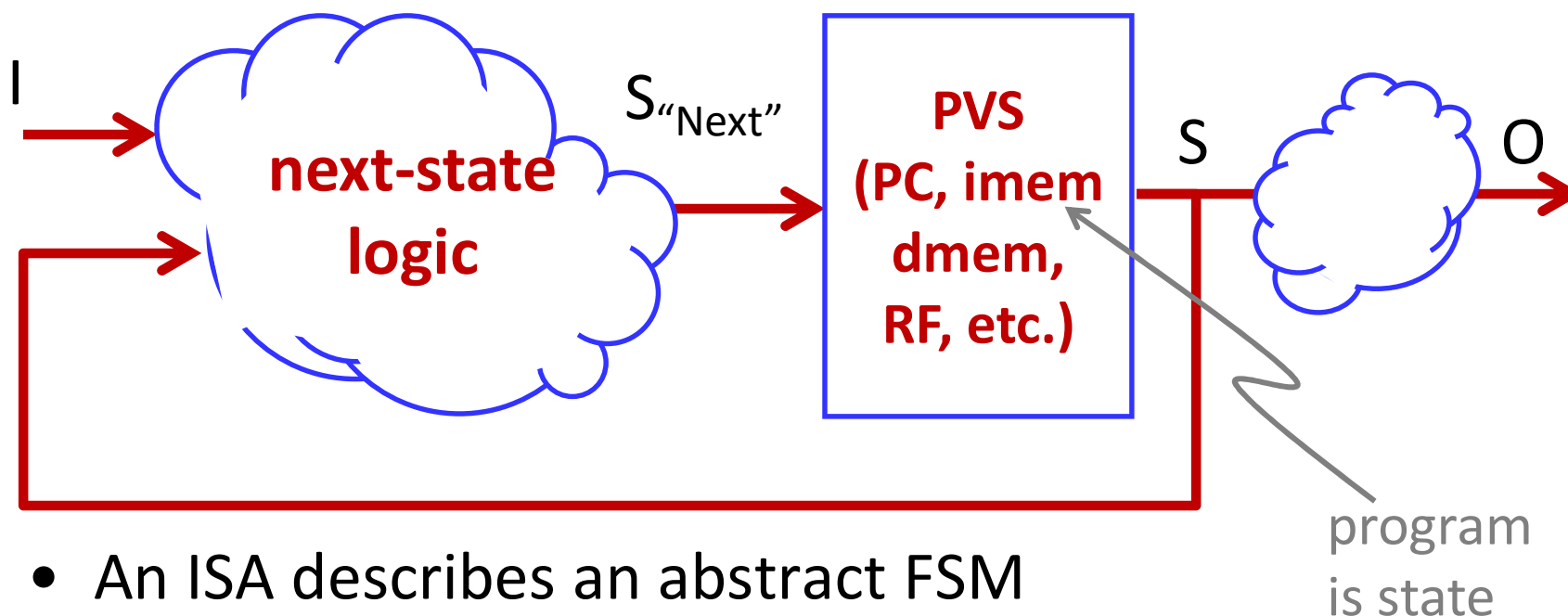

- An ISA describes an abstract FSM
  - state = program visible state
  - state transition = instruction execution
- Nice ISAs have atomic instruction semantics
  - one state transition per instruction in abstract FSM
- The implementation FSM can look wildly different
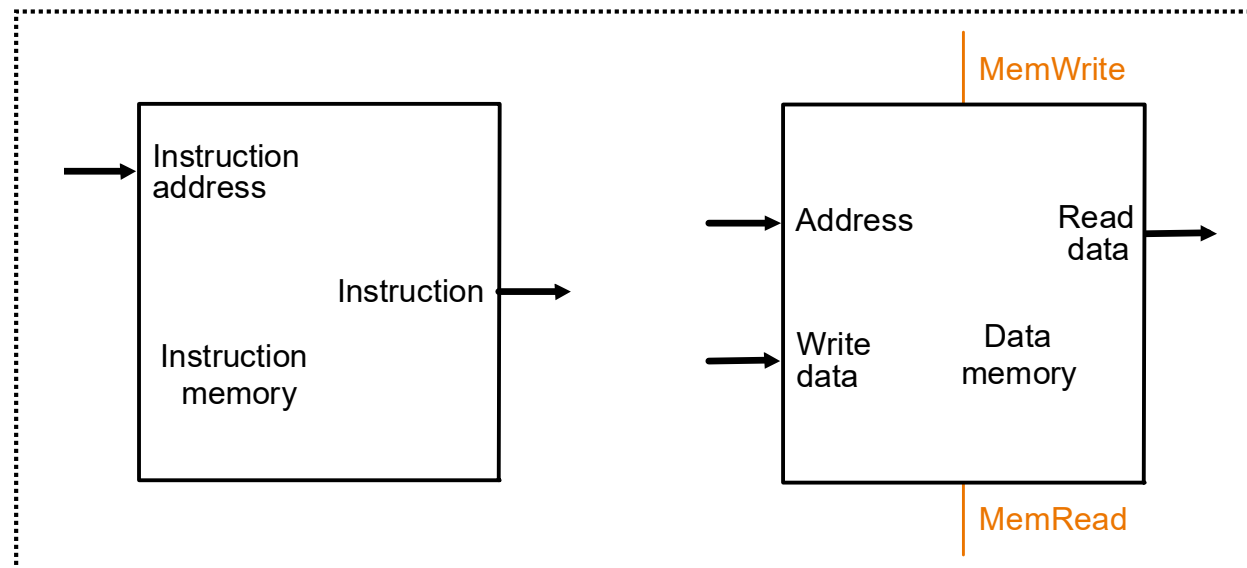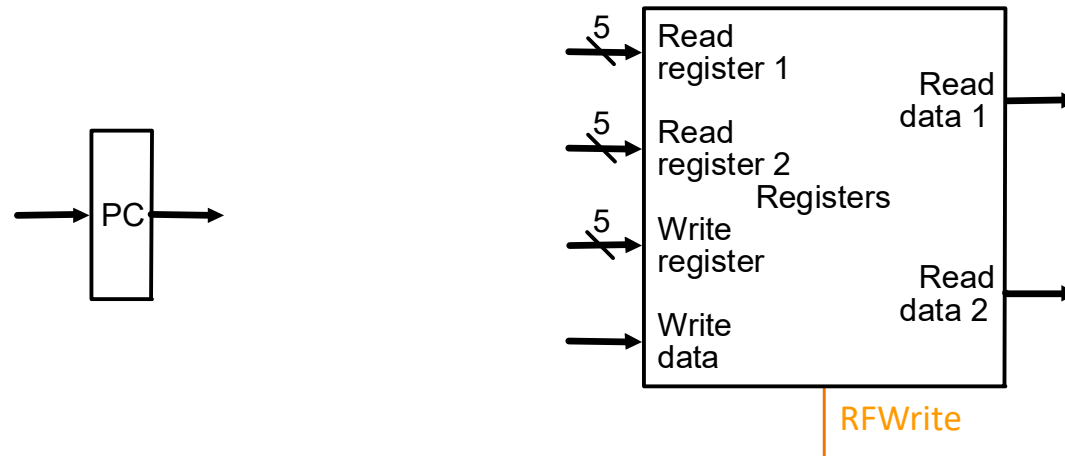
# Program Visible State (aka Architectural State)



*think  
interfaces  
not  
modules*

\*\*Based on original figure from [P&H CO&D, COPYRIGHT 2004 Elsevier. ALL RIGHTS RESERVED.]

# “Magic” Memory and Register File

- Combinational Read
    - output of the read data port is a combinational function of the register file contents and the corresponding read select port
  - Synchronous write
    - the selected register (or memory location) is updated on the posedge clock transition when write enable is asserted
- Cannot affect read output in between clock edges


# Simplifying Characteristics of “RISC”

- Simple ALU operations
  - 2-input, 1-output arithmetic and logical operations
  - few alternatives for accomplishing the same thing
- Simple data movements
  - ALU ops are register-to-register, never memory
  - “load-store” architecture, 1 addressing mode
- Simple branches
  - limited varieties of branch conditions and targets
  - PC-offset
- Simple instruction encoding
  - all instructions encoded in the same number of bits
  - simple, fixed formats

**(RISC=Reduced Instruction Set Computer)**
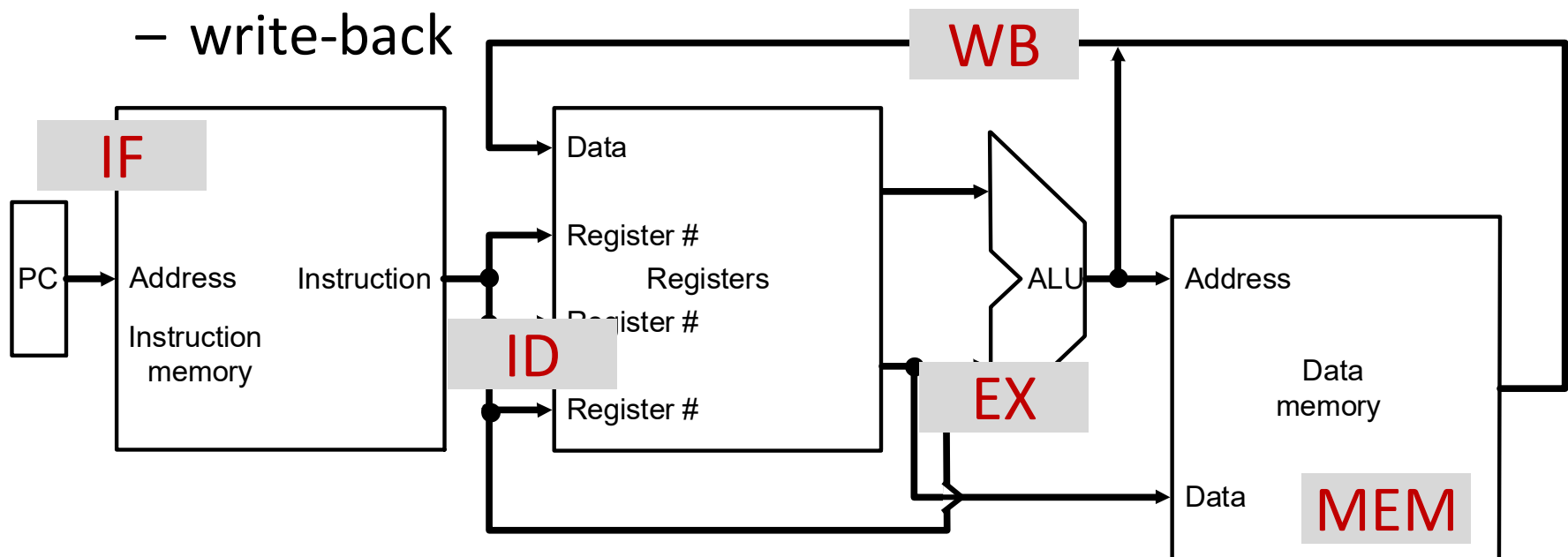
# RISC Instruction Processing

- 5 generic steps
  - instruction fetch
  - instruction decode and operand fetch
  - ALU/execute
  - memory access (not required by non-mem instructions)
  - write-back



# Single-Cycle Datapath for RV32I ALU Instructions



# Register-Register ALU Instructions

- Assembly (e.g., register-register addition)


**ADD** rd, rs1, rs2

- Machine encoding

0000000	rs2	rs1	000	rd	0110011
7-bit	5-bit	5-bit	3-bit	5-bit	7-bit

- Semantics
  - $\text{GPR}[\text{rd}] \leftarrow \text{GPR}[\text{rs1}] + \text{GPR}[\text{rs2}]$
  - $\text{PC} \leftarrow \text{PC} + 4$
- Exceptions: none (ignore carry and overflow)
- Variations
  - Arithmetic: {ADD, SUB}
  - Compare: {signed, unsigned} x {Set if Less Than}
  - Logical: {AND, OR, XOR}
  - Shift: {Left, Right-Logical, Right-Arithmetic}

# ADD rd rs1 rs2

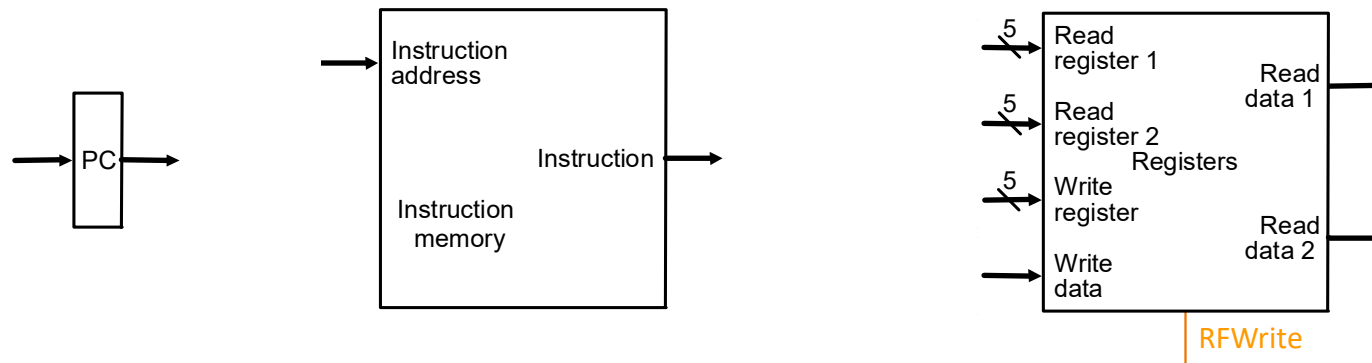

0000000	rs2	rs1	000	rd	0110011
7-bit	5-bit	5-bit	3-bit	5-bit	7-bit


```

if MEM[PC] == ADD rd rs1 rs2
    GPR[rd] ← GPR[rs1] + GPR[rs2]
    PC ← PC + 4
  
```



Combinational  
state update logic

# R-Type ALU Datapath

 

\*\*Based on original figure from [P&H CO&D, COPYRIGHT 2004 Elsevier. ALL RIGHTS RESERVED.]

# Reg-Immediate ALU Instructions

- Assembly (e.g., reg-immediate additions)


**ADDI** rd, rs1, imm<sub>12</sub>

- Machine encoding

imm[11:0]	rs1	000	rd	0010011
12-bit	5-bit	3-bit	5-bit	7-bit

- Semantics
  - $\text{GPR}[\text{rd}] \leftarrow \text{GPR}[\text{rs1}] + \text{sign-extend}(\text{imm})$
  - $\text{PC} \leftarrow \text{PC} + 4$
- Exceptions: none (ignore carry and overflow)
- Variations
  - Arithmetic: {ADDI, ~~SUBI~~}
  - Compare: {signed, unsigned} x {Set if Less Than Imm}
  - Logical: {ANDI, ORI, XORI}
  - \*\*Shifts by unsigned imm[4:0]: {SLLI, SRLI, SRAI}

# ADDI rd rs1 immediate<sub>12</sub>

 


imm[11:0]	rs1	000	rd	0010011
12-bit	5-bit	3-bit	5-bit	7-bit

if MEM[PC] == ADDI rd rs1 immediate  
 GPR[rd]  $\leftarrow$  GPR[rs1] + sign-extend (immediate)  
 PC  $\leftarrow$  PC + 4

IF	ID	EX	MEM	WB
----	----	----	-----	----

Combinational  
state update logic

# Datapath for R and I-type ALU Inst's

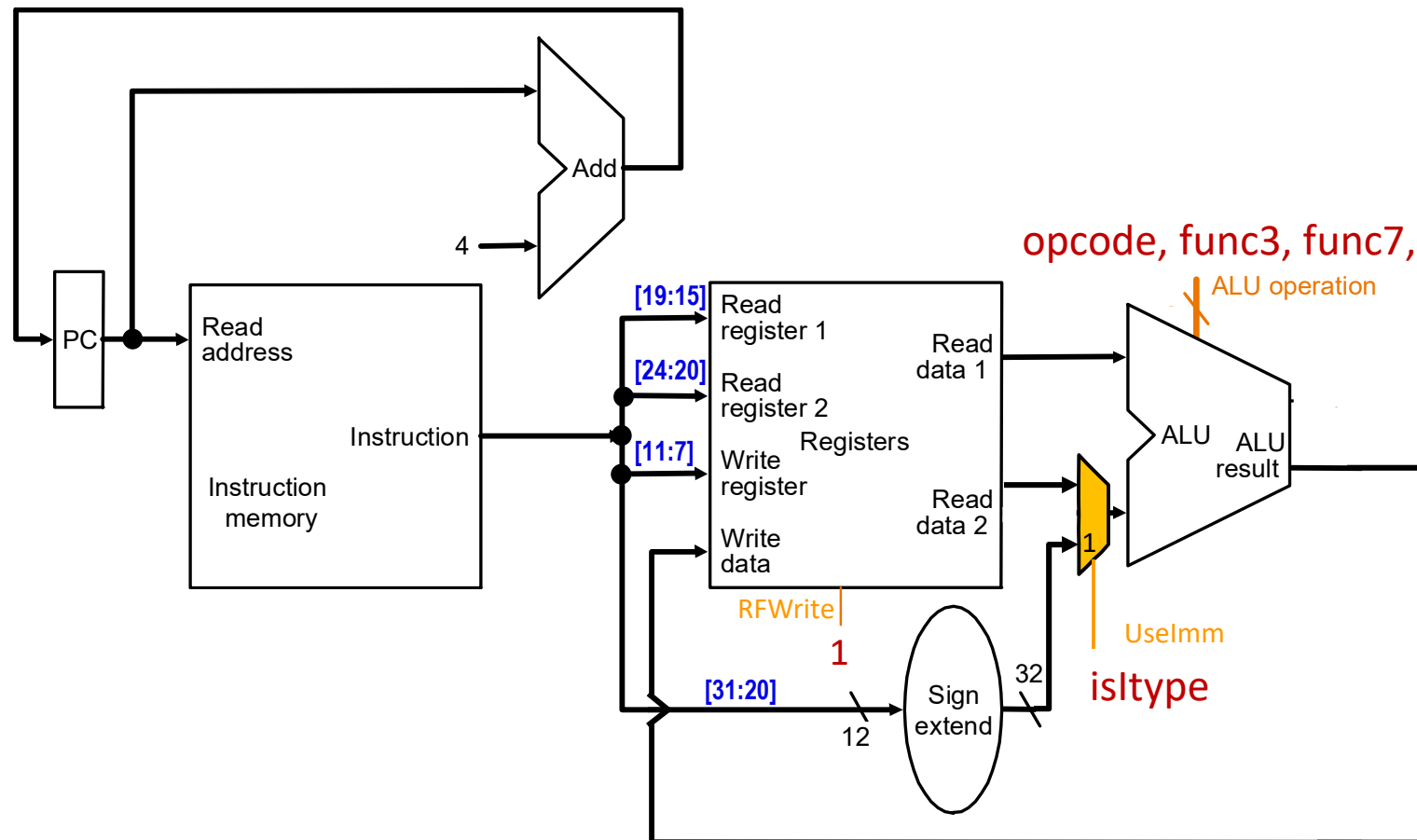

\*\*Based on original figure from [P&H CO&D, COPYRIGHT 2004 Elsevier. ALL RIGHTS RESERVED.]

# **Single-Cycle Datapath for Data Movement Instructions (i.e., Loads and Stores)**


# Load Instructions

- Assembly (e.g., load 4-byte word)

**LW** **rd**, **offset<sub>12</sub>**(**base**)

**rs1**

- Machine encoding

 

- Semantics

- $\text{byte\_address}_{32} = \text{sign-extend}(\text{offset}_{12}) + \text{GPR}[\text{base}]$
- $\text{GPR}[\text{rd}] \leftarrow \text{MEM}_{32}[\text{byte\_address}]$
- $\text{PC} \leftarrow \text{PC} + 4$

- Exceptions: none for now

- Variations: LW, LH, LHU, LB, LBU


e.g., LB ::  $\text{GPR}[\text{rd}] \leftarrow \text{sign-extend}(\text{MEM}_8[\text{byte\_address}])$

LBU ::  $\text{GPR}[\text{rd}] \leftarrow \text{zero-extend}(\text{MEM}_8[\text{byte\_address}])$

**Note: RV32I memory is byte-addressable, little-endian**



# LW Datapath

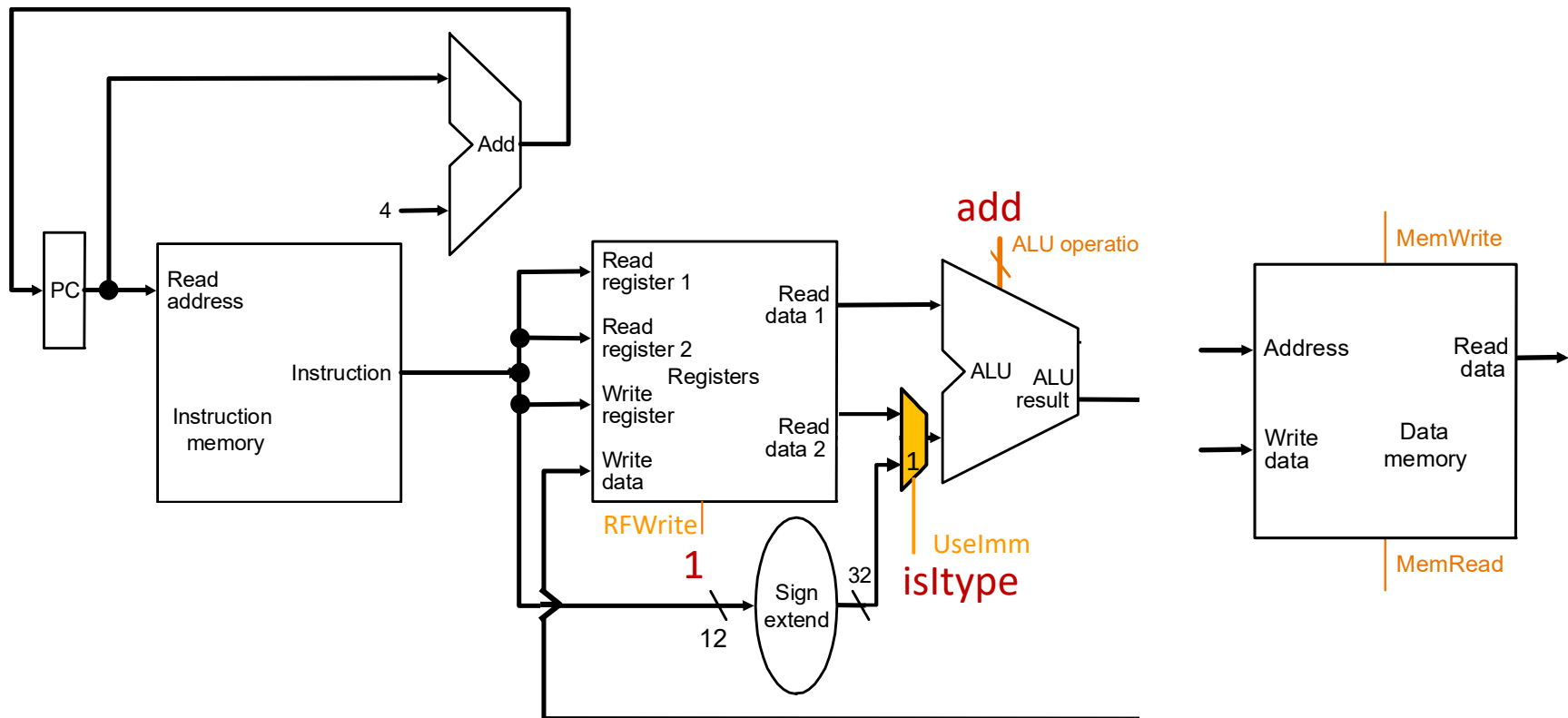

if  $\text{MEM}[\text{PC}] == \text{LW rd offset}_{12}(\text{base})$   
 $\text{EA} = \text{sign-extend}(\text{offset}) + \text{GPR}[\text{base}]$   
 $\text{GPR}[\text{rd}] \leftarrow \text{MEM}[\text{EA}]$   
 $\text{PC} \leftarrow \text{PC} + 4$

IF	ID	EX	MEM	WB
----	----	----	-----	----

Combinational  
state update logic

# Store Instructions

- Assembly (e.g., store 4-byte word)

**SW**  $rs2, offset_{12}(base)$


- Machine encoding

offset[11:5]	rs2	base	010	ofst[4:0]	0100011
7-bit	5-bit	5-bit	3-bit	5-bit	7-bit

- Semantics
  - $byte\_address_{32} = \text{sign-extend}(offset_{12}) + GPR[base]$
  - $MEM_{32}[byte\_address] \leftarrow GPR[rs2]$
  - $PC \leftarrow PC + 4$
- Exceptions: none for now
- Variations: SW, SH, SB

e.g., SB::  $MEM_8[byte\_address] \leftarrow (GPR[rs2])[7:0]$

# SW Datapath

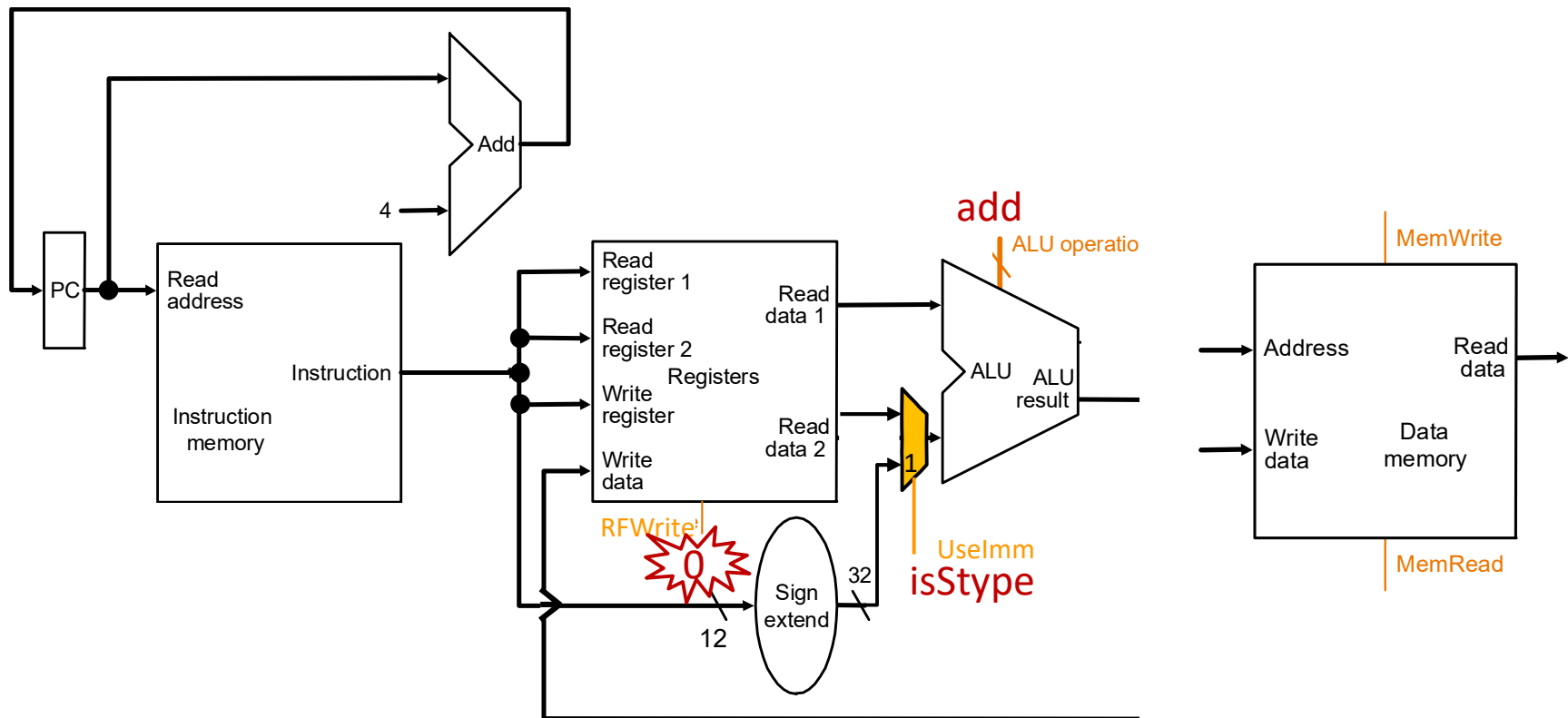


```

if MEM[PC] == SW rs2 offset12(base)
    EA = sign-extend(offset) + GPR[base]
    MEM[ EA ] ← GPR[rs2]
    PC ← PC + 4
  
```


IF	ID	EX	MEM	WB
----	----	----	-----	----

Combinational  
state update logic

# Load-Store Datapath

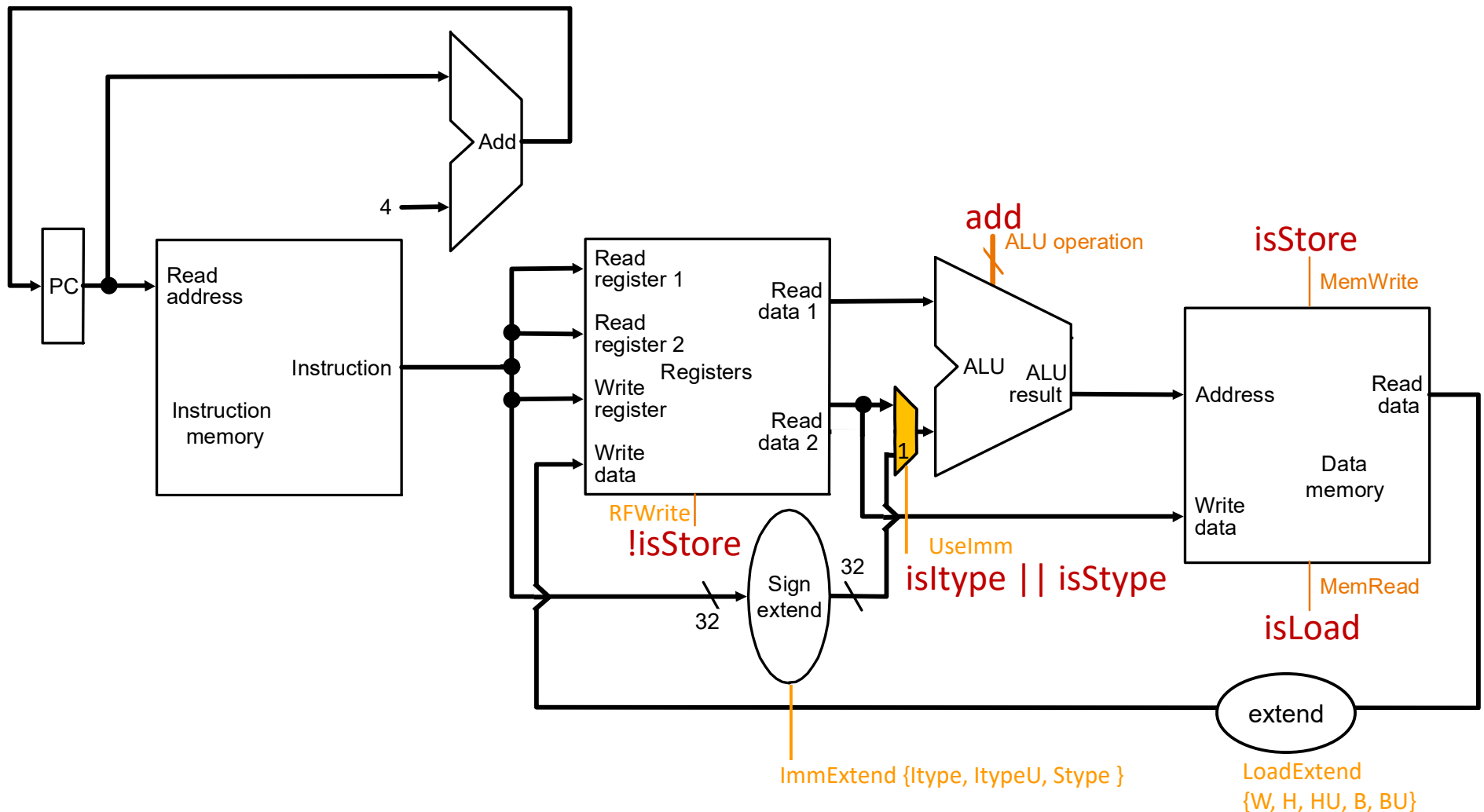

# Datapath for Non-Control Flow Inst's

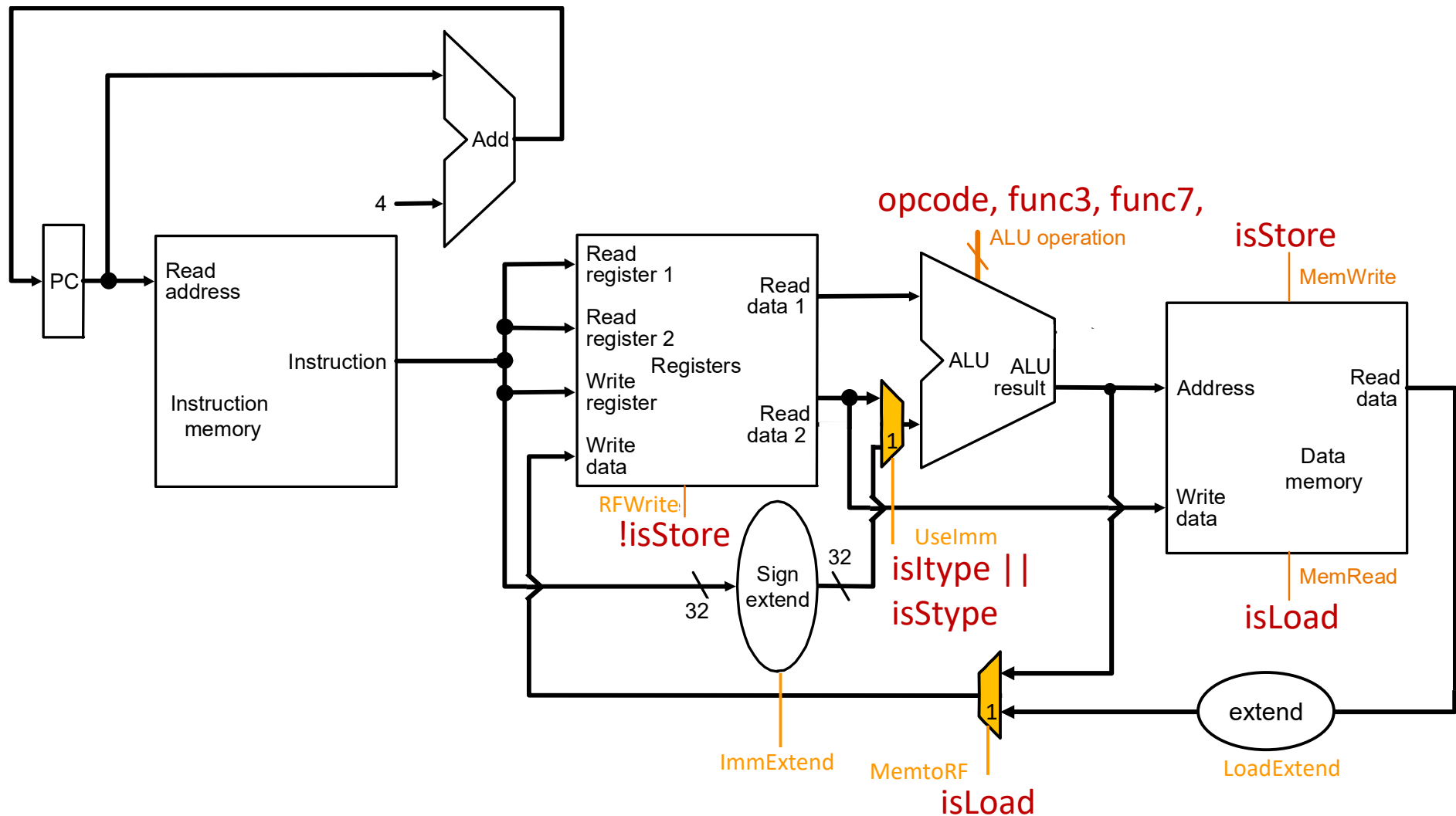

# Single-Cycle Datapath for Control Flow Instructions


# Jump and Link Instruction

- Assembly

**JAL** *rd* *imm*<sub>21</sub>

Note: implicit *imm*[0]=0

- Machine encoding

 

- Semantics

– target = PC + sign-extend(*imm*<sub>21</sub>)


– GPR[*rd*] ← PC + 4

– PC ← target

How far can you jump?

- Exceptions: misaligned target (4-byte)

# Unconditional Jump Datapath

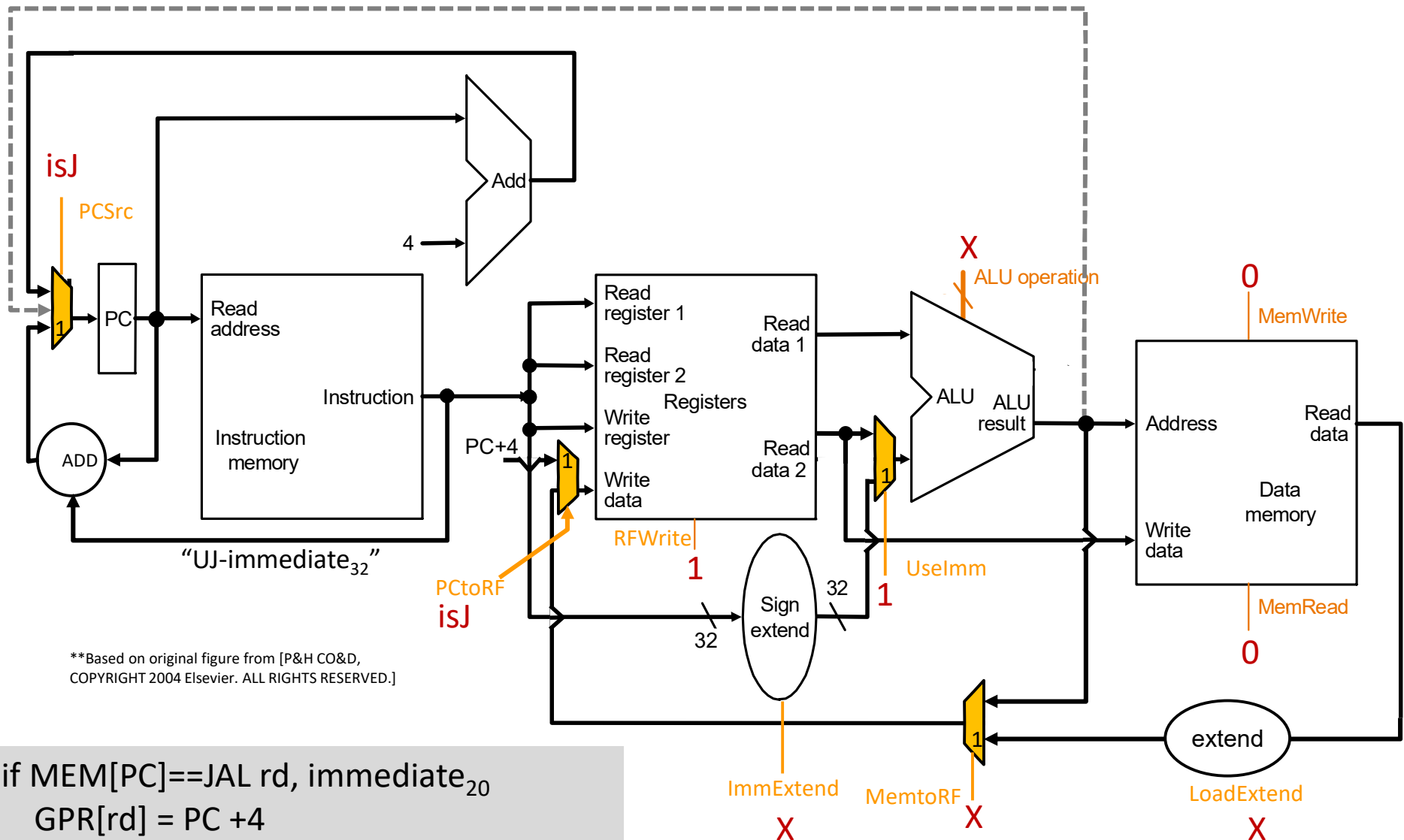

\*\*Based on original figure from [P&H CO&D,  
 COPYRIGHT 2004 Elsevier. ALL RIGHTS RESERVED.]

What about JALR?




# (Conditional) Branch Instructions

- Assembly (e.g., branch if equal)

**BEQ** *rs1*, *rs2*, *imm*<sub>13</sub>

**Note:** implicit *imm*[0]=0

- Machine encoding

 

- Semantics

– target = PC + sign-extend(*imm*<sub>13</sub>)


– if GPR[*rs1*]==GPR[*rs2*]                      then    PC ← target  
    else    PC ← PC + 4

**How far can you jump?**


- Exceptions: misaligned target (4-byte) if taken
- Variations
  - BEQ, BNE, BLT, BGE, BLTU, BGEU

# Conditional Branch Datapath

JAL and taken Branch

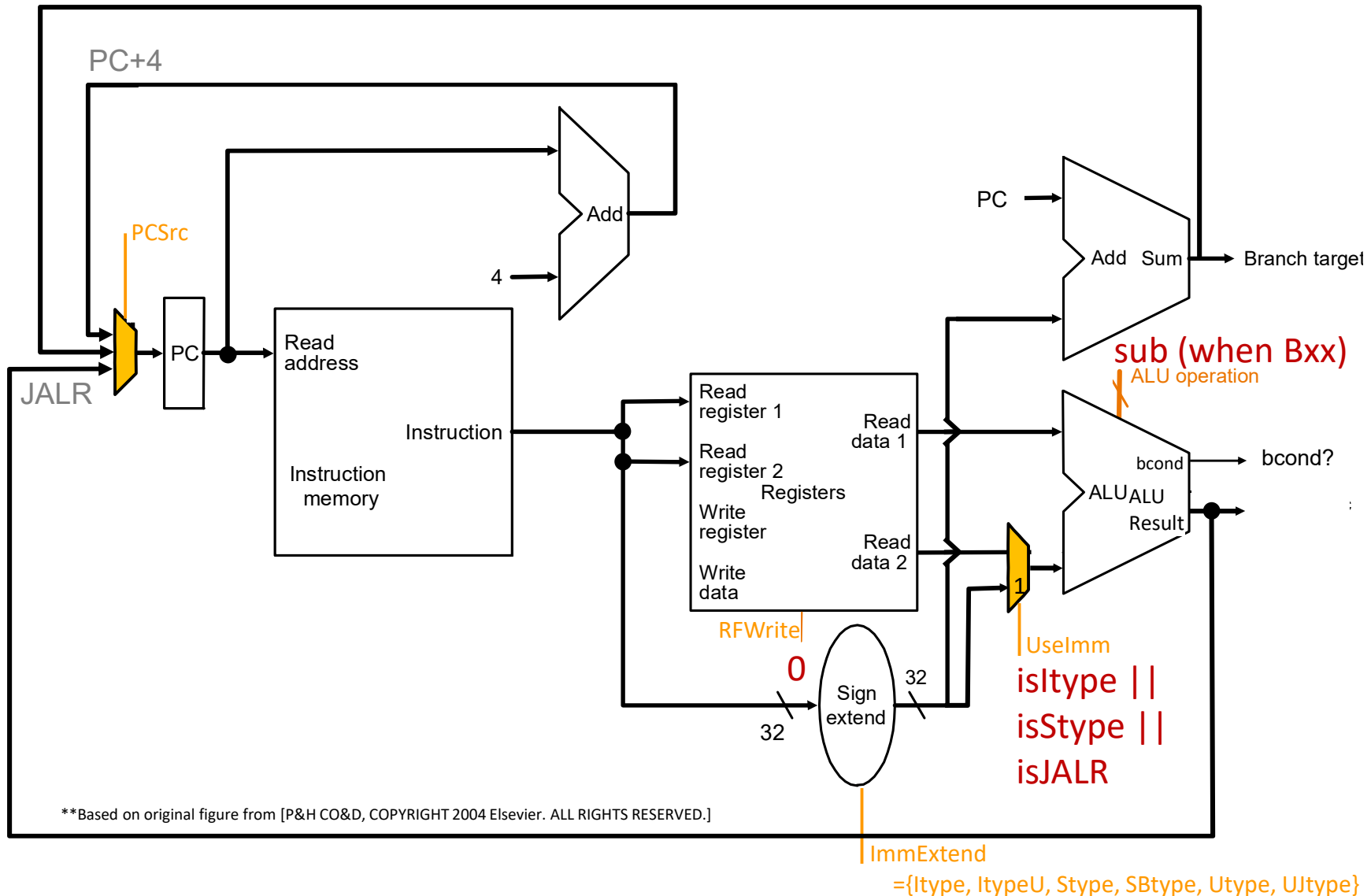


# Adding Control to Datapath

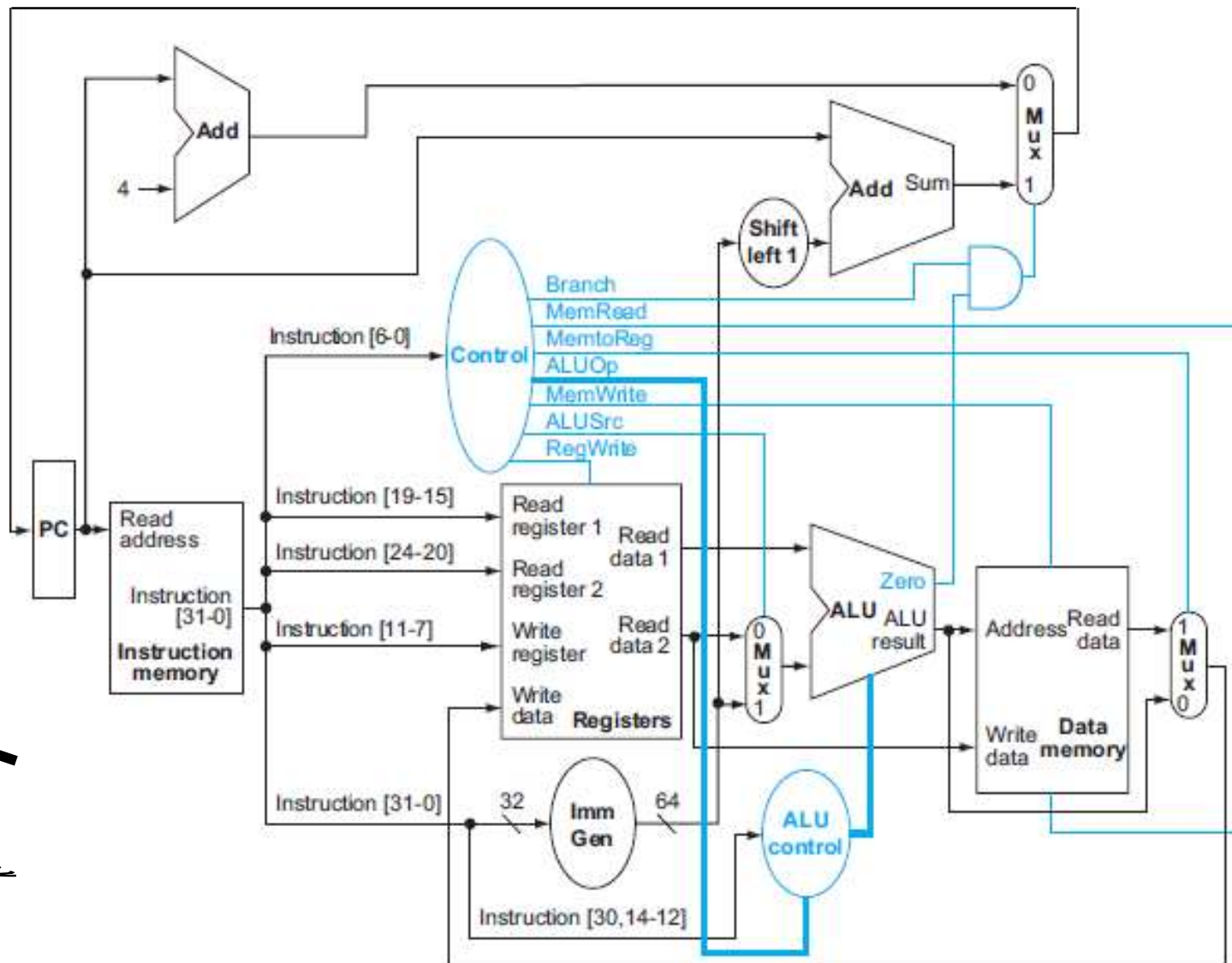


[Figure 4.17 from book, Copyright © 2018 Elsevier Inc. All rights reserved.]

# Datapath Control Generation

 


# R-Type ALU Worksheet:

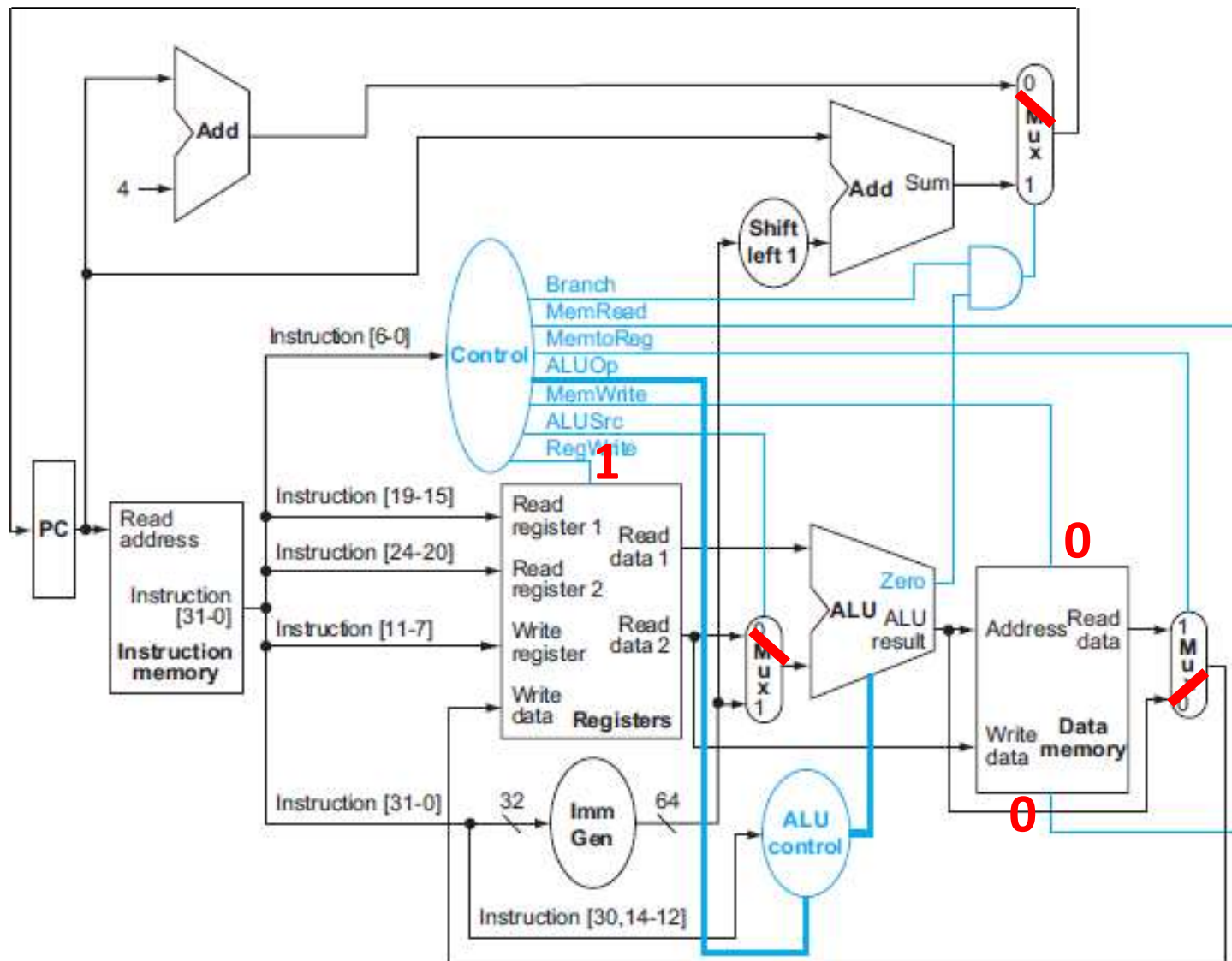


[Figure 4.17 from book, Copyright © 2018 Elsevier Inc. All rights reserved.]

# I-Type ALU Worksheet:

 


[Figure 4.17 from book, Copyright © 2018 Elsevier Inc. All rights reserved.]

# LW Worksheet:

 

[Figure 4.17 from book, Copyright © 2018 Elsevier Inc. All rights reserved.]


# SW Worksheet:

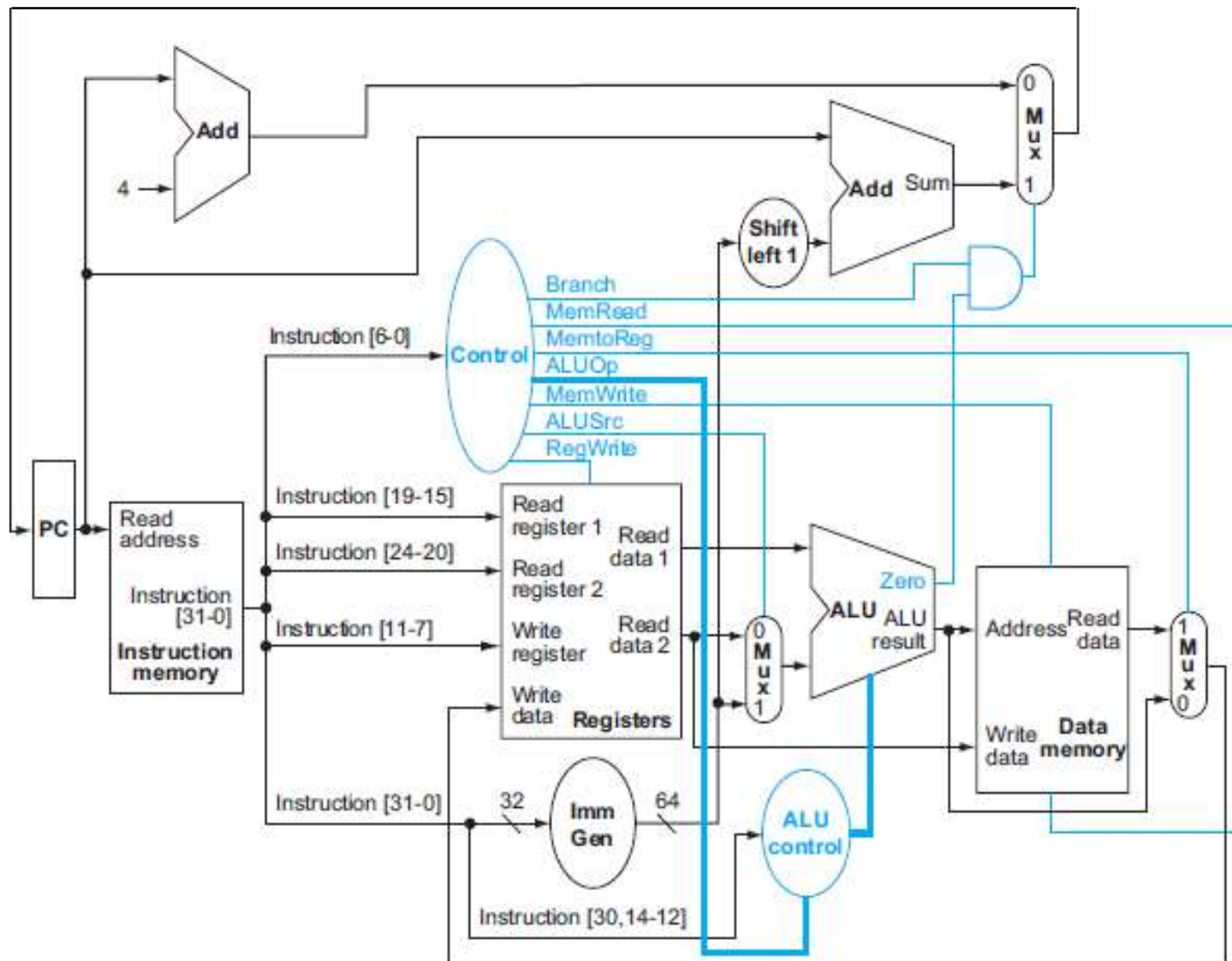

[Figure 4.17 from book, Copyright © 2018 Elsevier Inc. All rights reserved.]




# Branch Taken Worksheet:

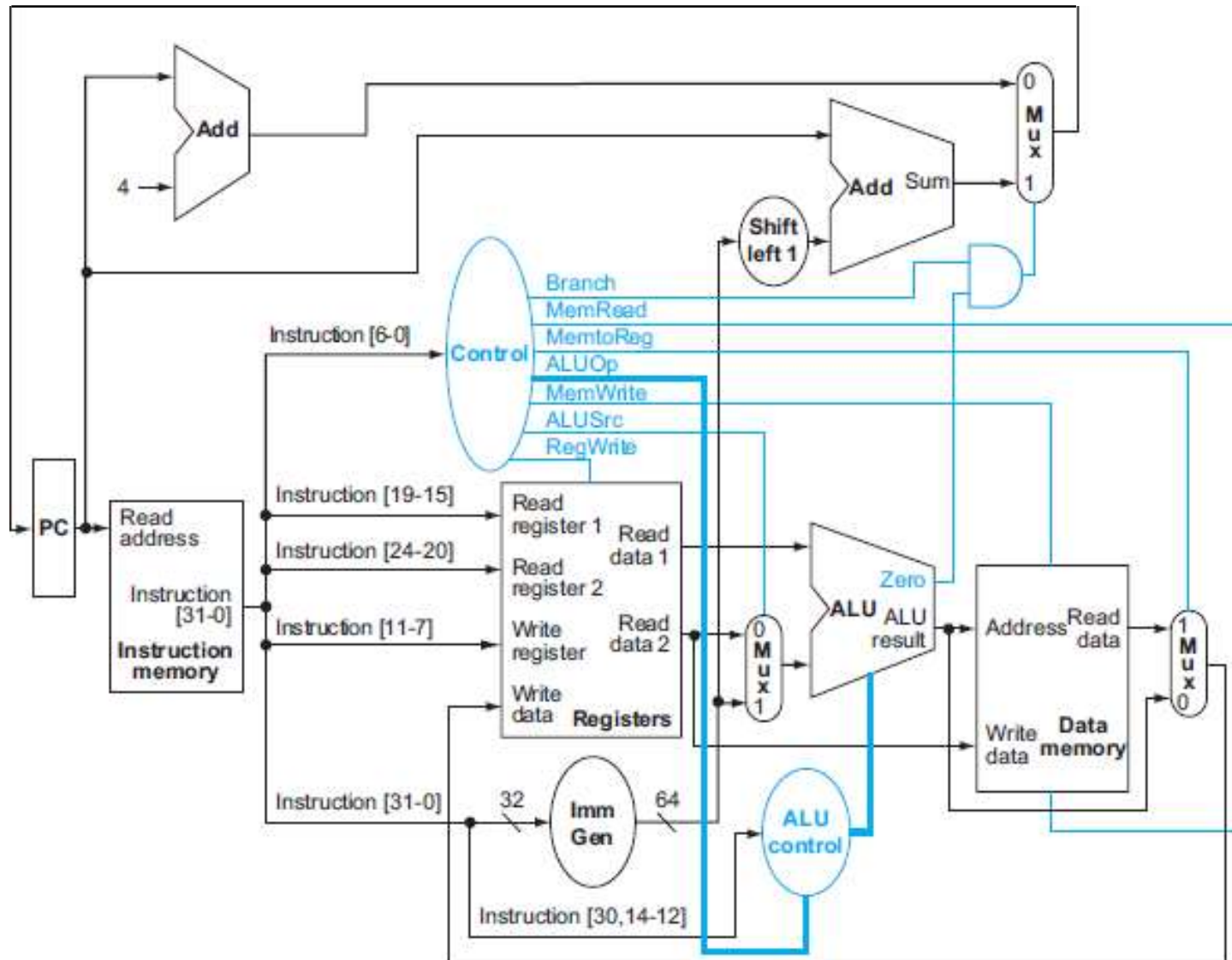


[Figure 4.17 from book, Copyright © 2018 Elsevier Inc. All rights reserved.]

# Branch Not-Taken Worksheet:

 

[Figure 4.17 from book, Copyright © 2018 Elsevier Inc. All rights reserved.]

# Jump (and Link?) ALU Worksheet:

 

[Figure 4.17 from book, Copyright © 2018 Elsevier Inc. All rights reserved.]

# Single-Bit Control Signals

	When De-asserted	When asserted	Equation
UseImm	2 <sup>nd</sup> ALU input from 2 <sup>nd</sup> GPR read port	2 <sup>nd</sup> ALU input from immediate	$(\text{opcode} \neq \text{IsRtype}) \ \&\& \ (\text{opcode} \neq \text{isBtype})$
RFWrite	GPR write disabled	GPR write enabled	$(\text{opcode} \neq \text{SW}) \ \&\& \ (\text{opcode} \neq \text{Bxx})$
MemtoRF	Steer ALU result to GPR write port	steer memory load to GPR write port	$\text{opcode} == \text{LW/H/B}$
PCtoRF	Steer above result to GPR write port	Steer PC+4 to GPR write port	$(\text{opcode} == \text{JAL}) \ \text{II} \ (\text{opcode} == \text{JALR})$
MemRead	Memory read disabled	Memory read port return load value	$\text{opcode} == \text{LW/H/B}$
MemWrite	Memory write disabled	Memory write enabled	$\text{opcode} == \text{SW/H/B}$

# Multi-Bit Control Signals

	Options	Equation
ALU Op	<ul style="list-style-type: none"> <li>ADD, SUB, AND, OR, XOR, NOR, LT, and Shift</li> <li>bcond: EQ, NE, GE, LT</li> </ul>	case opcode RTypeALU: according to funct3, funct7[5] ITypeALU : according to funct3 only (except shift) LW/SW/JALR : ADD Bxx : SUB and select bcond function — : ??
ImmExtend	Itype, ItypeU, Stype, SBtype, Utype, UJtype	<ul style="list-style-type: none"> <li>select based on instruction format type</li> <li>(may want to have separate extension units for primary ALU and PC-offset adder)</li> </ul>
PCSrc	PC+4, PCadder, ALU	case opcode JAL : PC + immediate JALR : GPR + immediate Bxx : taken?(PC + immediate):(PC + 4) — : PC+4
LoadExtend	W,H,HU,B,BU	case func3 . . . .

# Architecture vs Microarchitecture

Architecture

- Architectural Level



a clock has a hour hand and a minute hand, .....



a computer does ....?????....

You can read a clock without knowing how it works

conceptual

Microarchitecture

- Microarchitecture Level



a particular clockwork has a certain set of gears arranged in a certain configuration



a particular computer design has a certain datapath and a certain control logic

- Realization Level



machined alloy gears vs stamped sheet metal



CMOS vs ECL vs vacuum tubes

physical

# Special Notices about Labs

- Lab 1 fully rolling
  - RISC-V simulator (C code)
  - single-cycle RISC-V (RTL Verilog)
- To get yourself rolling **(even if waitlisted)**
  - get a GitHub account
  - find lab partners
- Please observe
  - lab assignments MUST be done in groups of 2 or 3
  - entire group MUST be present during check-off
  - 10% per day penalty for late labs, capped at 50%
  - **all labs MUST be checked off to pass the course**